

**1811****Code : 15EE42T**Register  
Number

--	--	--	--	--	--	--	--	--	--

**IV Semester Diploma Examination, April/May-2019****ELECTRICAL MEASUREMENT & MEASURING  
INSTRUMENTS****Time : 3 Hours ]****[ Max. Marks : 100**

- Note :** (i) Answer any **six** questions from PART – A. Each question carries **5** marks.  
(ii) Answer any **seven** questions from PART – B. Each question carries **10** marks.

**PART – A**

1. Define Error and list the types of errors in instruments. 5
2. Define the following terms with respect to measuring instruments : 5
  - (a) precision
  - (b) accuracy
3. List the merits of PMMC Instruments. 5
4. A balanced 3-phase star connected load draws power from 400 V supply. The two wattmeters connected indicates  $W_1 = 6$  kw and  $W_2 = 4$  kw, Calculate power and power factor of the circuit. 5
5. Explain the measurement of unknown resistance by Wheatstone bridge. 5
6. Explain the measurement of unknown inductance by Maxwell's bridge. 5
7. State the advantages of digital meters. 5
8. Draw the block diagram of digital tri-vector meter. 5
9. Draw the block diagram of DC signal conditioning system. 5

**PART – B**

10. Explain the construction and operation of permanent magnet moving coil instrument with neat sketch. 10

11. (a) Explain range extension of ammeter. 5  
(b) Explain calibration of voltmeter using potentiometer. 5
12. (a) Design a shunt to extend the range of ammeter from 500 mA to 5 Amps. The meter has internal resistance of 18 ohms. 5  
(b) A voltmeter has a resistance of 20 k $\Omega$  when connected in series with an external resistance across 230 V. supply. The instrument reads 160 volts. What is the value of external resistance ? 5
13. Explain with neat diagram construction and working of electro-dynamo meter type wattmeter. 10
14. Explain with neat diagram construction and working of induction type single phase energy meter. 10
15. Explain the operation of digital multimeter with a block diagram. 10
16. (a) Explain the operation of digital tong tester with a block diagram. 7  
(b) Draw the block diagram of general digital instrument. 3
17. (a) Explain the construction and operation of Thermo-couple pyrometer with a neat sketch. 8  
(b) Expand LVDT and RVDT. 2
18. (a) Explain the operation of LVDT with a neat sketch. 8  
(b) List the applications of Piezoelectric transducers. 2
19. (a) Draw the block diagram of digital power factor meter. 5  
(b) What is pyrometer and mention its applications. 5